



1a) completed truth table of the 7-segment display decoder:

| hex number | binary number | binary encoding |
|------------|---------------|-----------------|
| 0          | 4'b0000       | 7'b100_0000     |
| 1          | 4'b0001       | 7'b111_1001     |
| 2          | 4'b0010       | 7'b010_0100     |
| 3          | 4'b0011       | 7'b011_0000     |
| 4          | 4'b0100       | 7'b001_1001     |
| 5          | 4'b0101       | 7'b100_0010     |
| 6          | 4'b0110       | 7'b000_0010     |
| 7          | 4'b0111       | 7'b111_1000     |
| 8          | 4'b1000       | 7'b000_0000     |
| 9          | 4'b1001       | 7'b001_0000     |
| A          | 4'b1010       | 7'b000_1000     |
| B          | 4'b1011       | 7'b000_0011     |
| C          | 4'b1100       | 7'b100_0110     |
| D          | 4'b1101       | 7'b010_0001     |
| E          | 4'b1110       | 7'b000_0110     |
| F          | 4'b1111       | 7'b000_1110     |

1b) Implemented module decoder → siehe src ( decoder.sv)

1c) Finished implementation of the module decoder\_de10\_lite → siehe src (decoder\_de10\_lite.sv)

  1d) Compiled modules in Quartus Prime and programmed the FPGA of a DE10-Lite board. Verified that the board shows the correct hexadecimal numbers in the display for all combinations of the switches. Provided evidence for the following hex-numbers 0, 5, B, and E in pictures:



2a) Implemented module that uses 4-Bit ripple carry adder to compute  $C[4:0] = B[3:0] + A[3:0]$   
 → siehe src (tiny\_calculator.sv)

2b) -Testbench for tiny calculator to check the right outputs for Table2 → siehe src (tiny\_calculator\_tb.sv)  
 -Completed Table2:

| SW[7:4] | SW[3:0] | HEX3[6:0] | HEX2[6:0] | HEX1[6:0] | HEX0[6:0] |
|---------|---------|-----------|-----------|-----------|-----------|
| 0000    | 0001    | 100_0000  | 111_1001  | 100_000   | 111_1001  |
| 0010    | 0110    | 100_0000  | 000_0000  | 010_0100  | 000_0010  |
| 0111    | 0101    | 100_0000  | 100_0110  | 111_1000  | 001_0010  |
| 1000    | 1000    | 111_1001  | 100_0000  | 000_0000  | 000_0000  |
| 11111   | 1111    | 111_1001  | 000_0110  | 000_1110  | 000_1110  |

2c) Compiled modules in Quartus Prime and programmed the FPGA of a DE10-Lite board.  
 Verified that the board shows the correct hexadecimal numbers for the configurations in Table2 (2b).  
 Provided evidence for each of the five configurations:



Aufgabenbearbeitung:

Aufgabe 1 → Rahaf, Christian, Cora

Aufgabe 2 → Rahaf, Christian, Cora